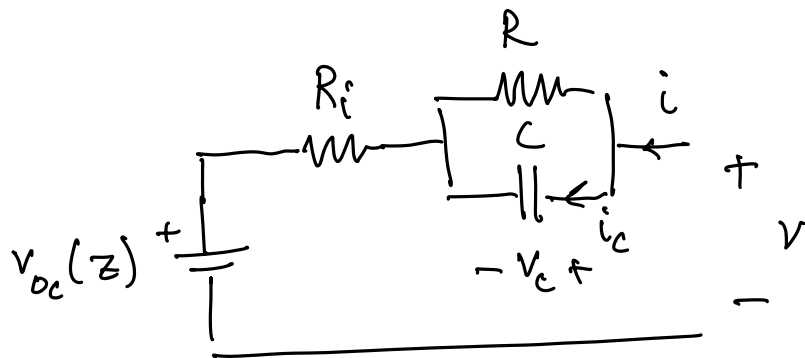


Derivation of an equivalent circuit model (ECM) in state-space form



$z = SOC$

states: z, v_c
input: i
output: v

KVL: $v = v_{oc}(z) + R_i i + v_c \quad (1)$

Capacitance: $i_c = C \cdot \frac{dv_c}{dt} \quad (2)$

eliminate i_c

KVL: $v_c = R(i - i_c) \quad (3)$

SOC: $z = \frac{1}{Q} \int i dt \Rightarrow \frac{dz}{dt} = \frac{1}{Q} \cdot i \quad (4)$

Solve i_c in (3): $v_c = Ri - Ri_c \Leftrightarrow Ri_c = Ri - v_c \Leftrightarrow i_c = i - \frac{v_c}{R}$

Substitute in (2):

$\frac{dv_c}{dt} = \frac{1}{C} \cdot i_c = \frac{1}{C} \left(i - \frac{v_c}{R} \right)$

ECM in ss-form

$\begin{cases} \frac{dv_c}{dt} = -\frac{v_c}{RC} + \frac{i}{C} \end{cases} \quad (5)$

$\begin{cases} \frac{dz}{dt} = \frac{1}{Q} \cdot i \end{cases} \quad (6)$


$\begin{cases} v = v_c + v_{oc}(z) + R_i i \end{cases} \quad (7)$

p20 Solving the model (5)(7) for a current step



Consider a current step:

$$i(t) = \begin{cases} 0 & t < 0 \\ I & t \geq 0 \end{cases}$$

$$v_c(0) = 0$$

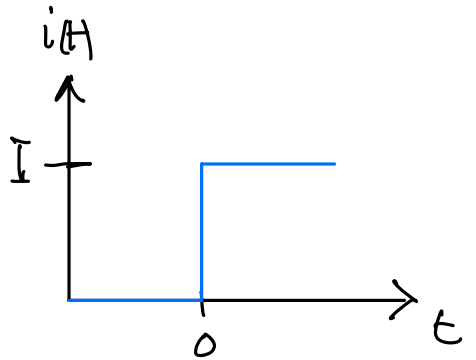

p21 Analytical solution for v_c and v :

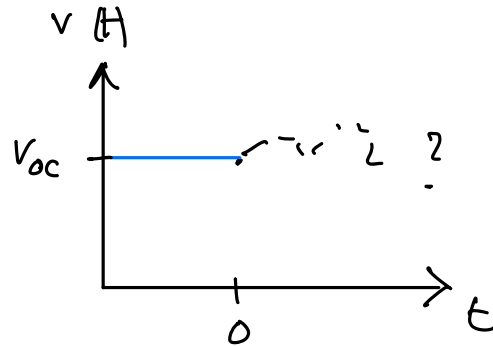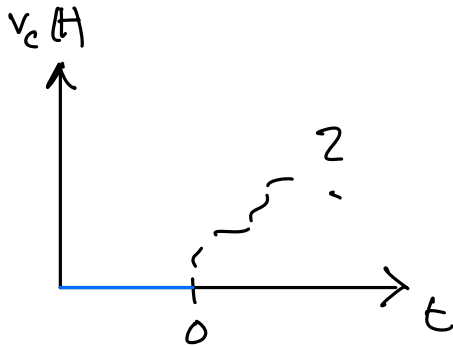

Equation (5) becomes the inhomogeneous differential eq

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = \frac{I}{C} \quad (t \geq 0) \quad (8)$$

The solution is

$$v_c = v_{c,h} + v_{c,p} \quad (9)$$

where $v_{c,h}$ is the general solution to $\frac{dv_c}{dt} + \frac{1}{RC} v_c = 0$

$$v_{c,h} = k e^{-\frac{1}{RC}t} \quad \frac{dv_{c,h}}{dt} = -\frac{1}{RC} \cdot k e^{-\frac{1}{RC}t} = -\frac{1}{RC} v_{c,h}$$

$v_{c,p}$ a particular solution to the inhomogeneous equation (8).

Choose $V_{c,p}$ to be a constant such that

$$\frac{1}{RC} \cdot V_{c,p} = \frac{I}{C} \Leftrightarrow V_{c,p} = RI$$

The solution (9) is

$$V_c = k e^{-\frac{1}{RC} \cdot t} + RI$$

k is computed from the initial condition $V_c(0) = 0$



$$0 = k \cdot \underbrace{e^0}_{=1} + RI \Leftrightarrow k = -RI$$

The solution of (8) is

$$V_c = RI(1 - e^{-\frac{1}{RC}t})$$

and from (7) we get:
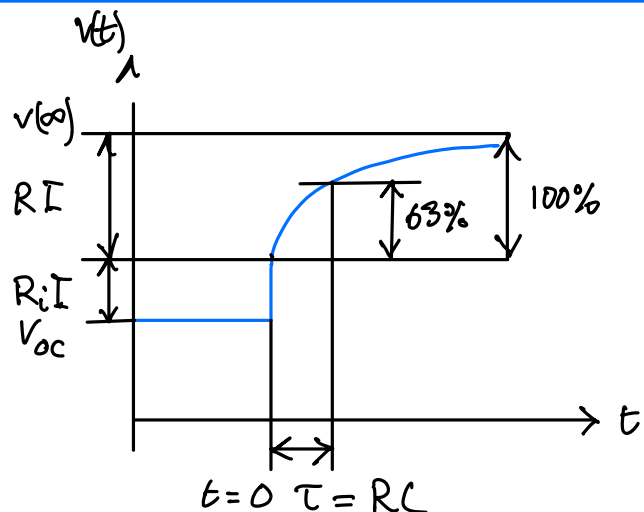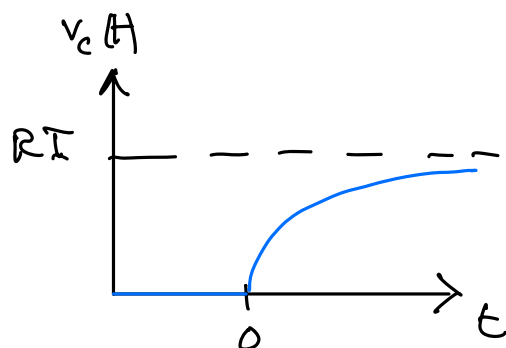
$$V = \begin{cases} V_{oc} + RI(1 - e^{-\frac{1}{RC}t}) + R_i I & t \geq 0 \\ V_{oc} & t < 0 \end{cases} \quad (10)$$



p22 Computation of model parameters (from step response)


Parameters: V_{oc} , R_i , R , C

V_{oc} : $V(0^-) = V_{oc}$

R_i : $V(0) = V_{oc} + R_i I$

$$V(0) - V_{oc} = R_i I$$

$$R_i = \frac{V(0) - V_{oc}}{I}$$

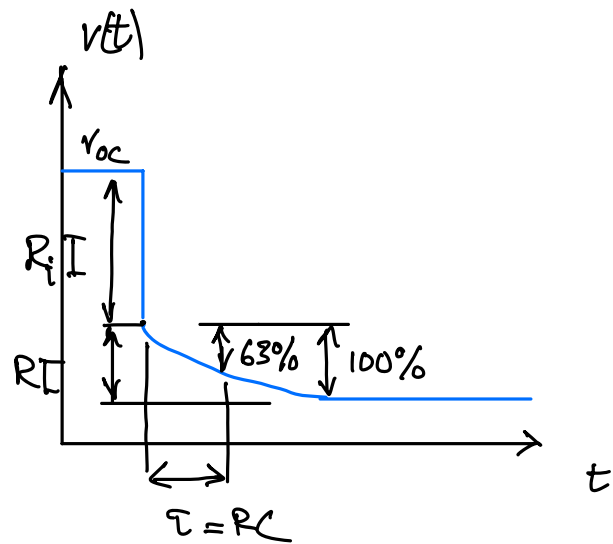

R : $V(\infty) = V_{oc} + RI + R_i I$

$$V(\infty) - (V_{oc} + R_i I) = RI$$

$$R = \frac{V(\infty) - (V_{oc} + R_i I)}{I}$$

C : The time constant τ of the system is the time $t = \tau$ it takes to reach $1 - e^{-1} = 63\%$ of the final value after a step input is applied.

τ is measured in the figure.

The exponent is -1 at $t = \tau$:

$$-1 = -\frac{1}{RC} \cdot \tau \Leftrightarrow \tau = RC \Leftrightarrow C = \frac{\tau}{R}$$

ECM in time discrete form

Time continuous form:

$$\begin{cases} \frac{dv_c(t)}{dt} = -\frac{v_c(t)}{RC} + \frac{i(t)}{C} \\ v(t) = v_c(t) + v_{oc} + R_i i(t) \end{cases}$$


Consider sampled signals:

$$x_k = x(t)$$

$$x_{k+1} = x(t + \Delta t)$$

$$x_{k+2} = x(t + 2\Delta t)$$

\vdots

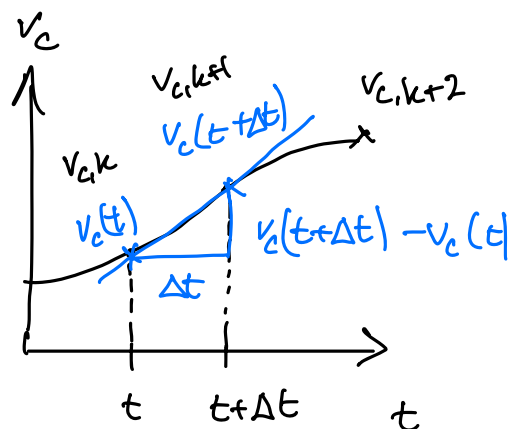

Euler forward approximation of the derivative:

$$\frac{dv_c}{dt}(t) \approx \frac{v_c(t + \Delta t) - v_c(t)}{\Delta t} = \frac{v_{c,k+1} - v_{c,k}}{\Delta t}$$

$$\begin{cases} \frac{v_{c,k+1} - v_{c,k}}{\Delta t} = -\frac{v_{c,k}}{RC} + \frac{i_k}{C} \\ v_k = v_{c,k} + v_{oc,k} + R_i i_k \end{cases}$$

$$\begin{cases} v_{c,k+1} = v_{c,k} \left(1 - \frac{\Delta t}{RC} \right) + \frac{i_k}{C} \Delta t \\ v_k = v_{c,k} + v_{oc,k} + R_i i_k \end{cases}$$

Linear Regression

Put the model

$$\left\{ \begin{array}{l} \frac{V_{c,k+1} - V_{c,k}}{\Delta t} = - \frac{V_{c,k}}{RC} + \frac{i_k}{C} \end{array} \right. \quad (11)$$

$$\left\{ \begin{array}{l} V_k = V_{c,k} + V_{oc,k} + R_i i_k \end{array} \right. \quad (12)$$

in the form

$Y = X\theta$ where Y, X are known matrices and θ parameters to be estimated.

Row k is expressed as

$$y_k = x_{k1}\theta_1 + x_{k2}\theta_2 + x_{k3}\theta_3$$

Let $\tilde{v}_k = v_k - v_{oc,k}$ to eliminate $v_{oc,k}$

$$(12) \Rightarrow \tilde{v}_k = v_{c,k} + R_i i_k \quad (12')$$

Eliminate $v_{c,k}, v_{c,k+1}$ in (11) and (12') :

Solve $v_{c,k}$ in (12') : $v_{c,k} = \tilde{v}_k - R_i i_k$

Substitute in (11) :

$$\frac{\tilde{v}_{k+1} - R_i i_{k+1} - (\tilde{v}_k - R_i i_k)}{\Delta t} = -\frac{1}{RC} (\tilde{v}_k - R_i i_k) + \frac{i_k}{C}$$

The linear regression is

$$\underbrace{\frac{\tilde{v}_{k+1} - \tilde{v}_k}{\Delta t}}_{= y_k} = \underbrace{R_i}_{\theta_1} \underbrace{\frac{i_{k+1} - i_k}{\Delta t}}_{x_{k1}} + \underbrace{\frac{1}{RC}}_{\theta_2} \underbrace{(-\tilde{v}_k)}_{x_{k2}} + \underbrace{\left(\frac{R_i}{RC} + \frac{1}{C}\right)}_{\theta_3} \underbrace{i_k}_{x_{k3}}$$

The matrices are

$$Y = \begin{bmatrix} \frac{\tilde{v}_2 - \tilde{v}_1}{\Delta t} \\ \vdots \\ \frac{\tilde{v}_h - \tilde{v}_{h-1}}{\Delta t} \end{bmatrix} \quad X = \begin{bmatrix} \frac{i_2 - i_1}{\Delta t} & -\tilde{v}_1 & i_1 \\ \vdots & \vdots & \vdots \\ \frac{i_n - i_{n+1}}{\Delta t} & -\tilde{v}_{n-1} & i_{n-1} \end{bmatrix}$$

In Matlab : $\Theta = X \backslash Y$

Model parameters can be computed by solving :

$$\begin{cases} \theta_1 = R_i \\ \theta_2 = \frac{1}{RC} \\ \theta_3 = \frac{R_i}{RC} + \frac{1}{C} \end{cases}$$

Solution :

$$\underline{R_i} : R_i = \theta_1$$

$$\underline{C} : \theta_3 = \theta_1 \cdot \theta_2 + \frac{1}{C} \Leftrightarrow C = (\theta_3 - \theta_1 \theta_2)^{-1}$$

$$\underline{R} : R = \frac{1}{C \theta_2} = \frac{\theta_3 - \theta_1 \theta_2}{\theta_2} = \frac{\theta_3}{\theta_2} - \theta_1$$