


Battery Modelling

TSFS19 Battery Systems - Lectures 3 and 4

Mattias Krysanter

Battery Modelling – Equivalent Circuit Models

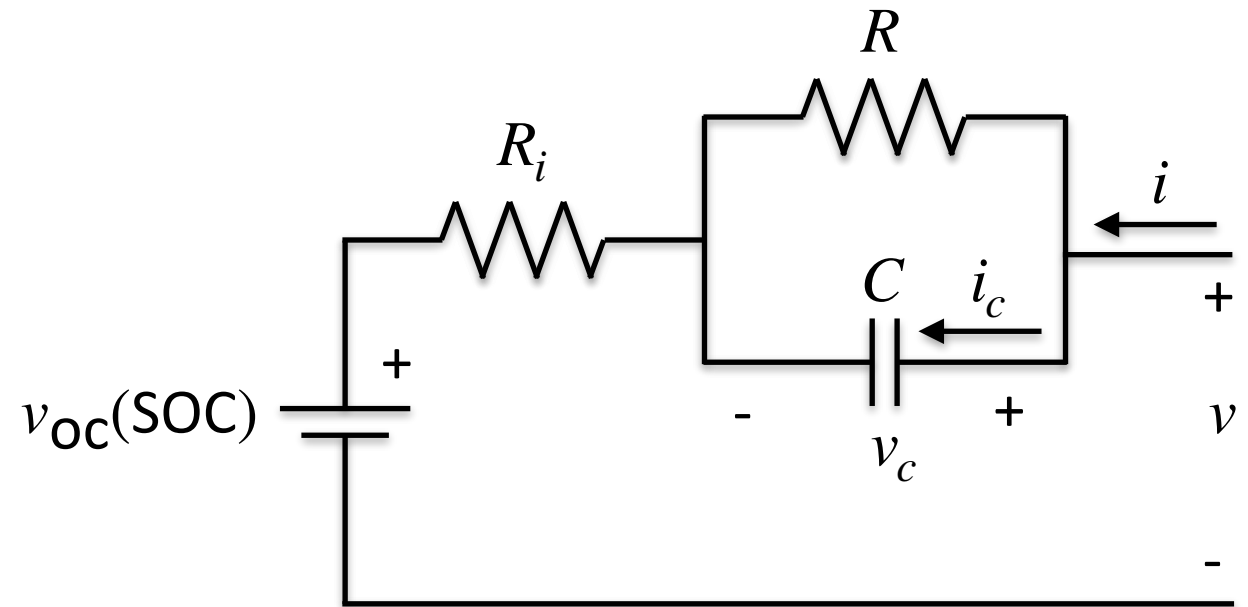
- Equivalent circuit model (ECM) describing the relationship between the voltage of the battery v and current i ($i > 0$ during charging)
- The model consists of 3 parts:
 - The charge capacity Q of the cell.
 - Open circuit voltage as a function of SOC, $v_{oc}(SOC)$
 - Battery impedance describing the polarization losses.
- The parts can be modeled separately using different measurements.



Battery Modelling Lectures – Content


- Show **typical experiments** used for parameterization.
- **Identify battery capacity** from measurements.
- Identify the **open circuit voltage as a function of SOC** from measurement data.
- Convert a time-continuous model into a time-discrete model
- **Identify battery impedance** from
 - a current step using voltage response characteristics.
 - dynamic operation using linear regression and non-linear minimization methods.
- **Assumptions:**
 - Impedance is constant, i.e., does not significantly depend on SOC.
 - The OCV is only dependent on SOC.
 - Temperature is fixed to 25°C, so temperature dependence need not be considered.
- This and the next lecture prepare for the first computer lab where an ECM will be developed from measurement data.

Capacity and Open Circuit Voltage

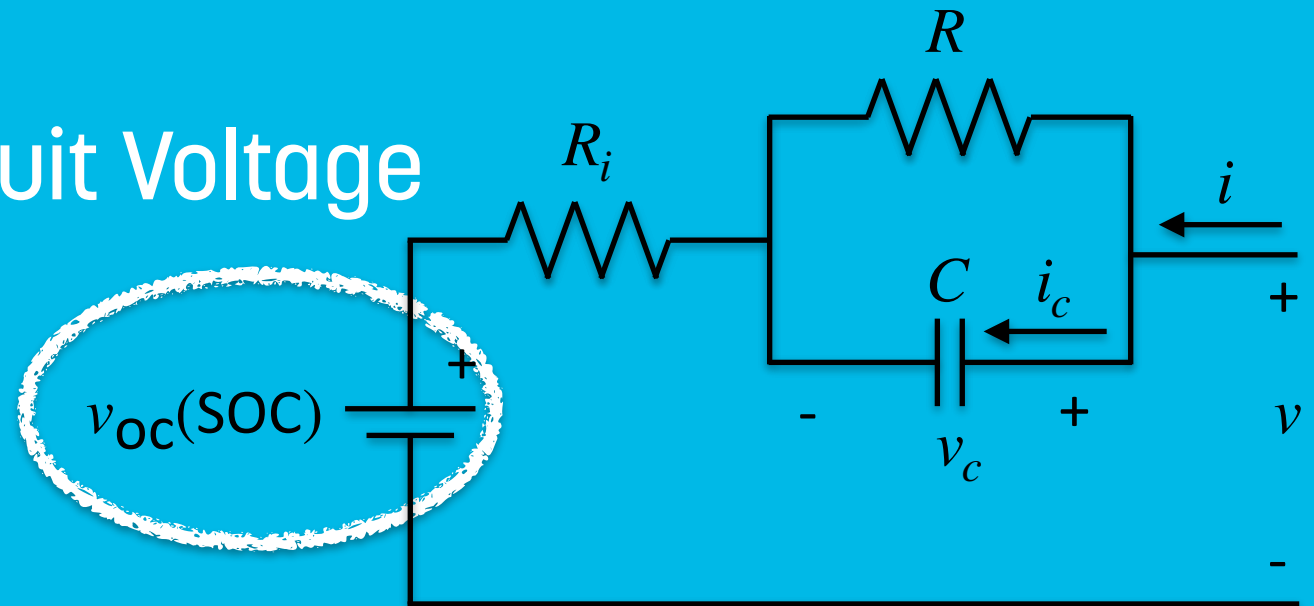

Open Circuit Voltage

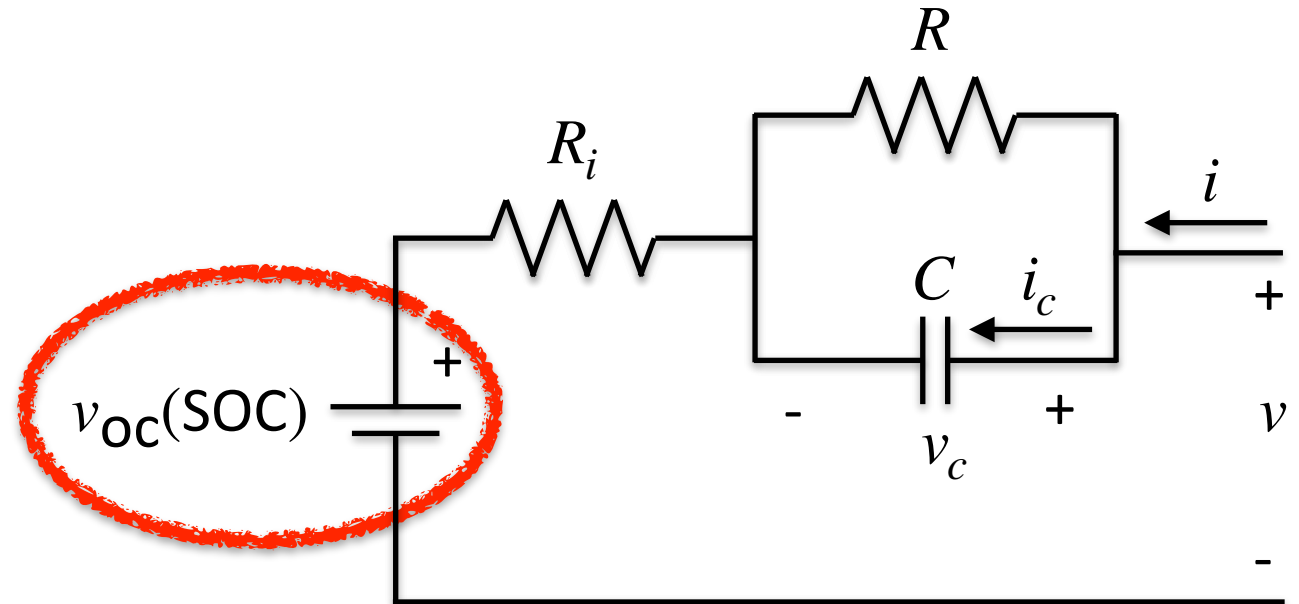
- Requirements for identifying OCV:
- Measurements from the entire SOC range, from fully charged to discharged battery.
- If the battery has rested ($i = 0$) long enough, $v_c = 0$ and $v_{oc}(SOC) = v$ which can be measured.
- To save time in measuring the OCV curve, it is usually sufficient to use a small current.



Capacity Estimation


- Definitions:
- The **capacity** is the amount of charge going from 0% SOC to 100% SOC.
- **0% SOC**: $OCV = V_{min}$ (the minimum allowed terminal voltage)
- **100% SOC**: $OCV = V_{max}$ (the maximum allowed terminal voltage)
- To get to 100%/0% SOC CCCV charge/discharge needs to be performed.
- A low current can be used to get close to 100%/0% SOC, the smaller the better.

SOC is not 100 % after CC-charging

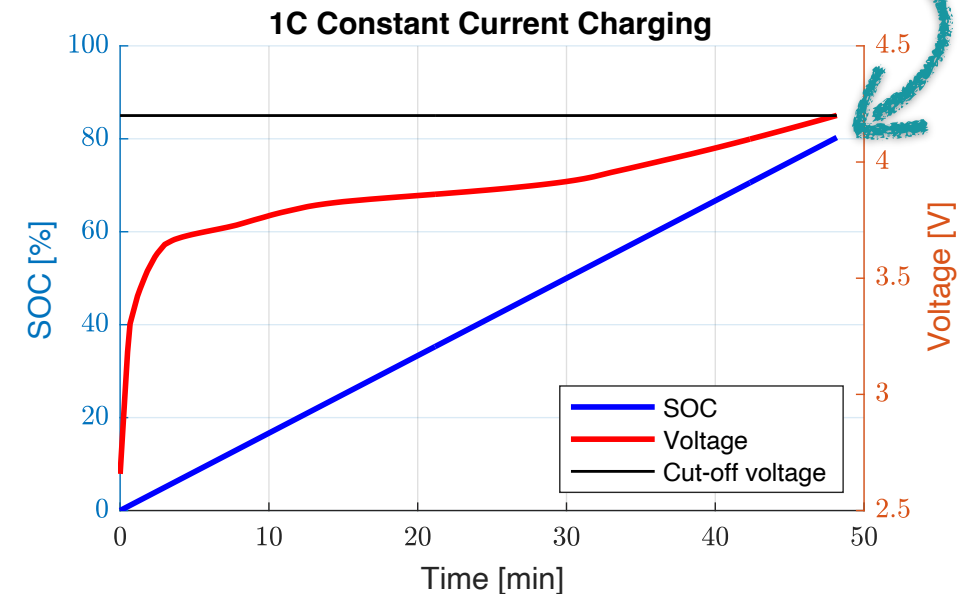

Cycling Test/Capacity Estimation

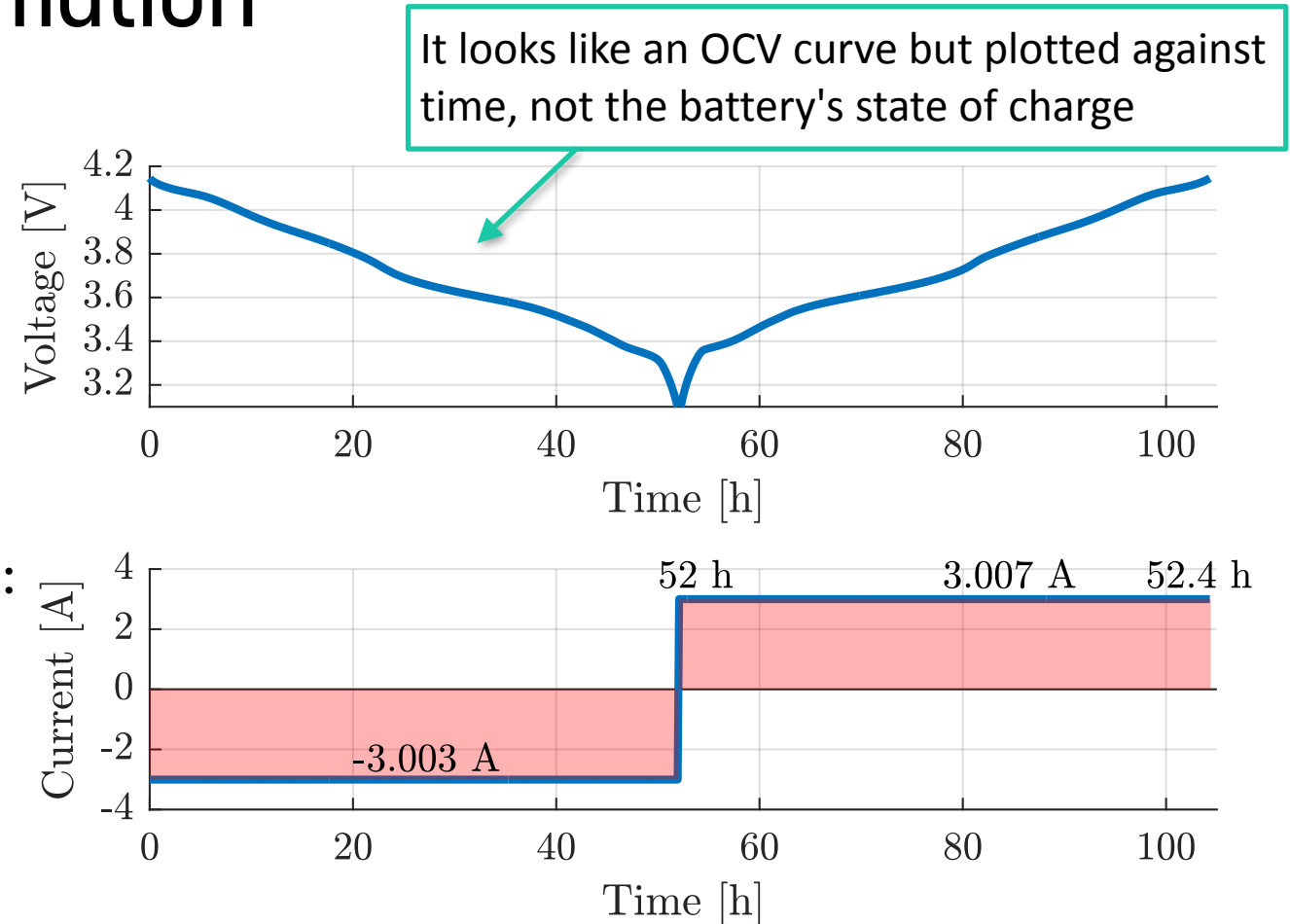
- Low current, here 3 A (C/50)
- Cycling
 - Discharge from maximum to minimum allowable voltage: 4.15 V- >3.1V
 - Charging: 3.1V->4.15V
- The (discharge) capacity can be calculated:
 - $Q = - \int_{\text{full}}^{\text{empty}} i dt = - I \Delta t =$
 - $= 3.003 \cdot 52 = 156.2 \text{ Ah}$



Numerical Integration: The trapezoidal rule


- Compute $\int_0^{\pi} \sin(x) dx =$
 $= [-\cos(x)]_0^{\pi} = 1 - (-1) = 2$
- Numerical approximation:
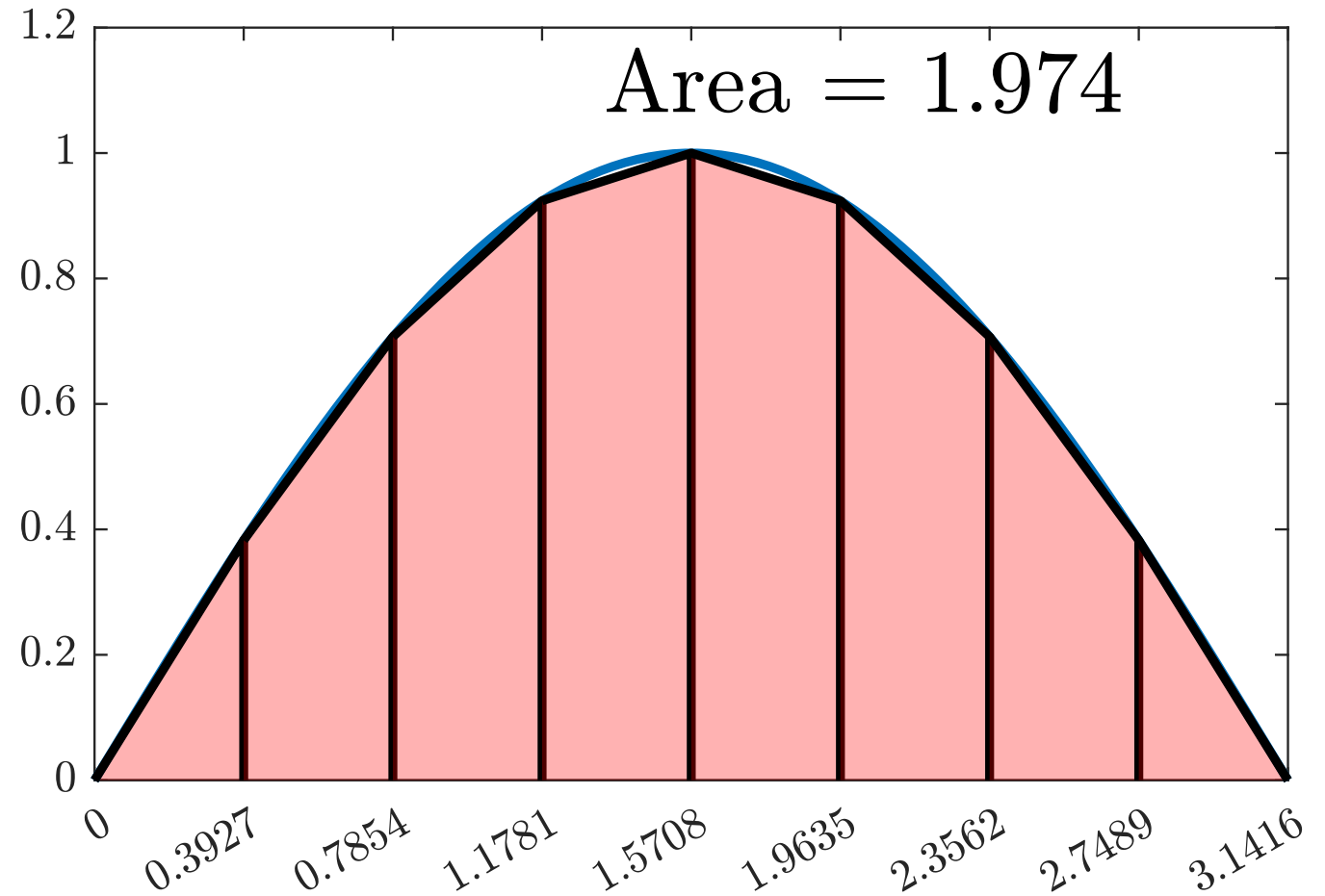
```
x = [0:pi/8:pi];  
y = sin(x);  
Area = trapz(x,y);
```



Voltage as a function of DoD

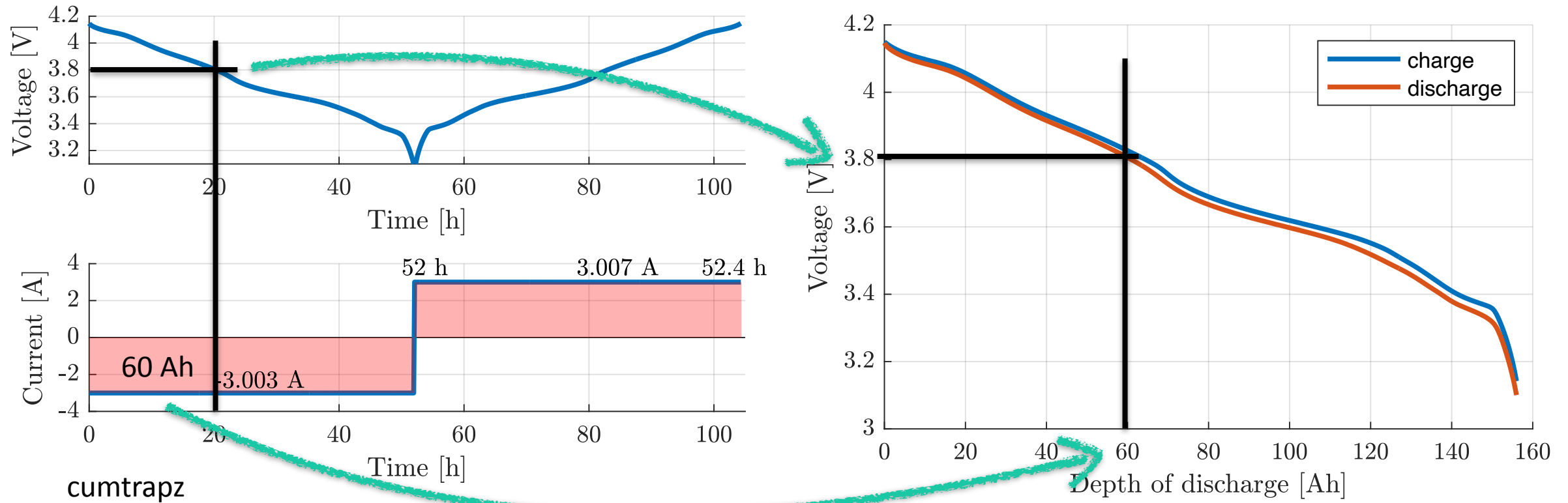- Illustration of voltage calculation as a function of DoD.



Relationship between SOC and DOD

SOC is defined, as you may recall, by

$$z = \frac{\text{remaining charge}}{\text{total capacity}}$$

This can be expressed with the battery's total capacity Q_{tot} and DoD as

$$z = \frac{Q_{\text{tot}} - \text{DoD}}{Q_{\text{tot}}}$$

Open Circuit Voltage (OCV)



For constant current $I_{\text{dis}} < 0$ and $I_{\text{chg}} > 0$ during discharge and charge, the following applies:

$$v_{\text{dis}}(z) = v_{\text{oc}}(z) + I_{\text{dis}}(R_i(z) + R(z))$$

$$v_{\text{chg}}(z) = v_{\text{oc}}(z) + I_{\text{chg}}(R_i(z) + R(z))$$

If $I_{\text{dis}} = -I_{\text{chg}}$ then OCV can be approximated by
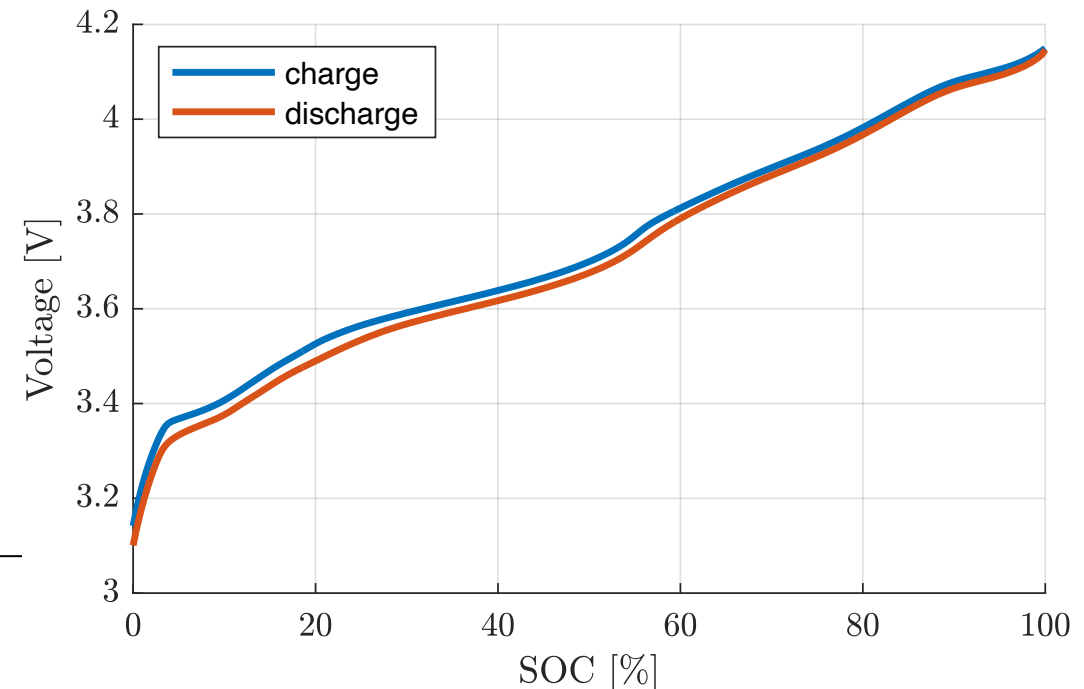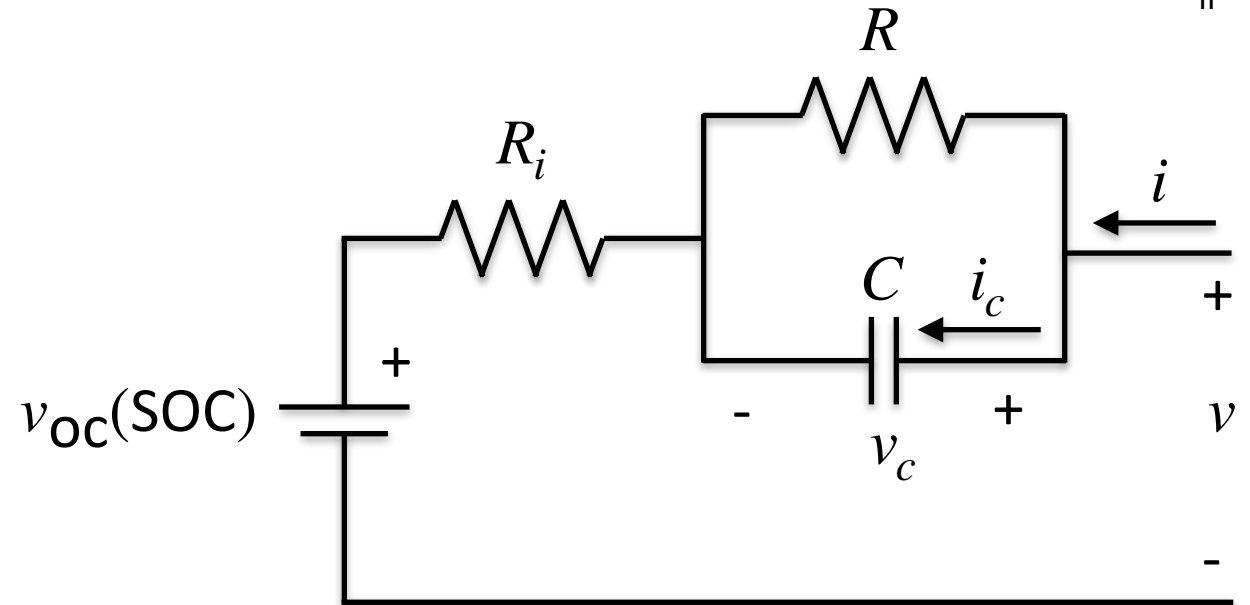
$$v_{\text{oc}}(z) \approx \frac{v_{\text{chg}}(z) + v_{\text{dis}}(z)}{2}$$



OCV-function for High SOC-values

- $v_{oc}(SOC) \approx \frac{v_{chg}(SOC) + v_{dis}(SOC)}{2}$ cannot be used for high SOC's, see figure.

- Assume the resistance is not changing much for high SOC's:

$$\tilde{R} = R_i(SOC) + R(SOC)$$

- From


$$v_{dis}(SOC) = v_{oc}(SOC) + I_{dis}\tilde{R}$$

$$v_{chg}(SOC) = v_{oc}(SOC) + I_{chg}\tilde{R}$$

we get

$$\tilde{R} = \frac{v_{chg}(SOC) - v_{dis}(SOC)}{I_{chg} - I_{dis}}$$

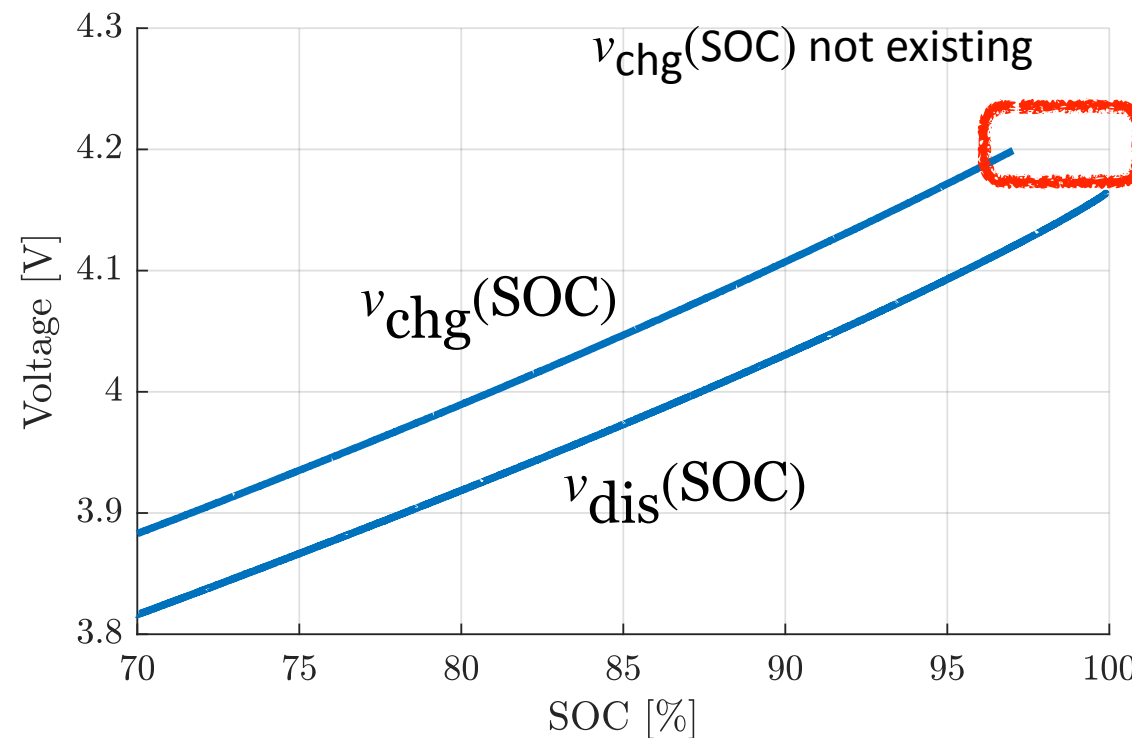- Compute \tilde{R} for a high SOC when both voltages exist.
- Estimate OCV as $v_{oc}(SOC) = v_{dis}(SOC) - I_{dis}\tilde{R}$
- Check also that $v_{oc}(100) = v_{cut-off}$



OCV-function Implementation

- In Matlab the OCV-function can be implemented as interpolation in a table as

```
% SOC = [0:0.01:1]; example SOC grid  
% OCV(i) is the open circuit voltage at SOC(i)  
OCVf = @(z) interp1(SOC,OCV,z)  
SOCf = @(v) interp1(OCV,SOC,v)
```


- Given a SOC-value z the OCV voltage ocv is computed as

```
ocv = OCVf(z)
```

- Given a open circuit voltage v the SOC-value soc is computed as


```
soc = SOCf(v)
```

Impedance Modeling

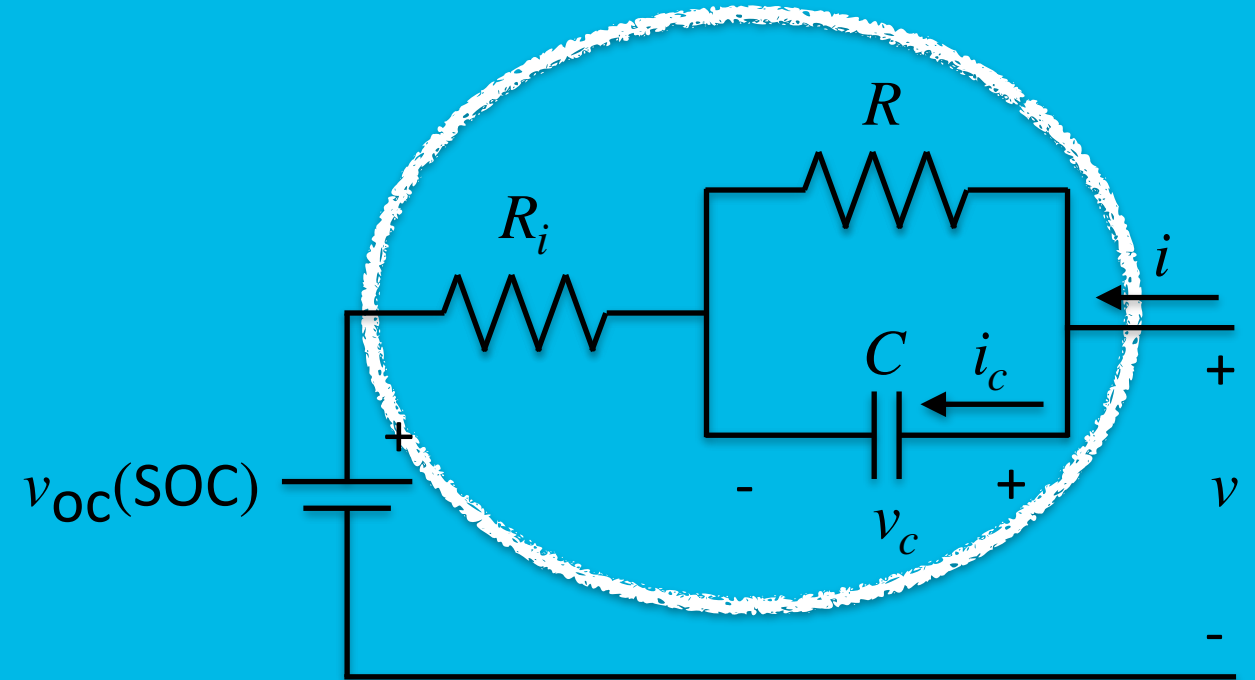

Impedance Estimation

- The impedance in this model depends on the parameters R_i , R , and C .
- The parameters can depend on SOC and temperature.
- Next, a method for estimating parameters for a given SOC and temperature is described.
- Identify the impedance using data where SOC does not change significantly.
- The current must vary to estimate the capacitance C .
- Here, a step in current is chosen, but sinusoidal waves at different frequencies or white noise with a broad frequency content are also commonly used.

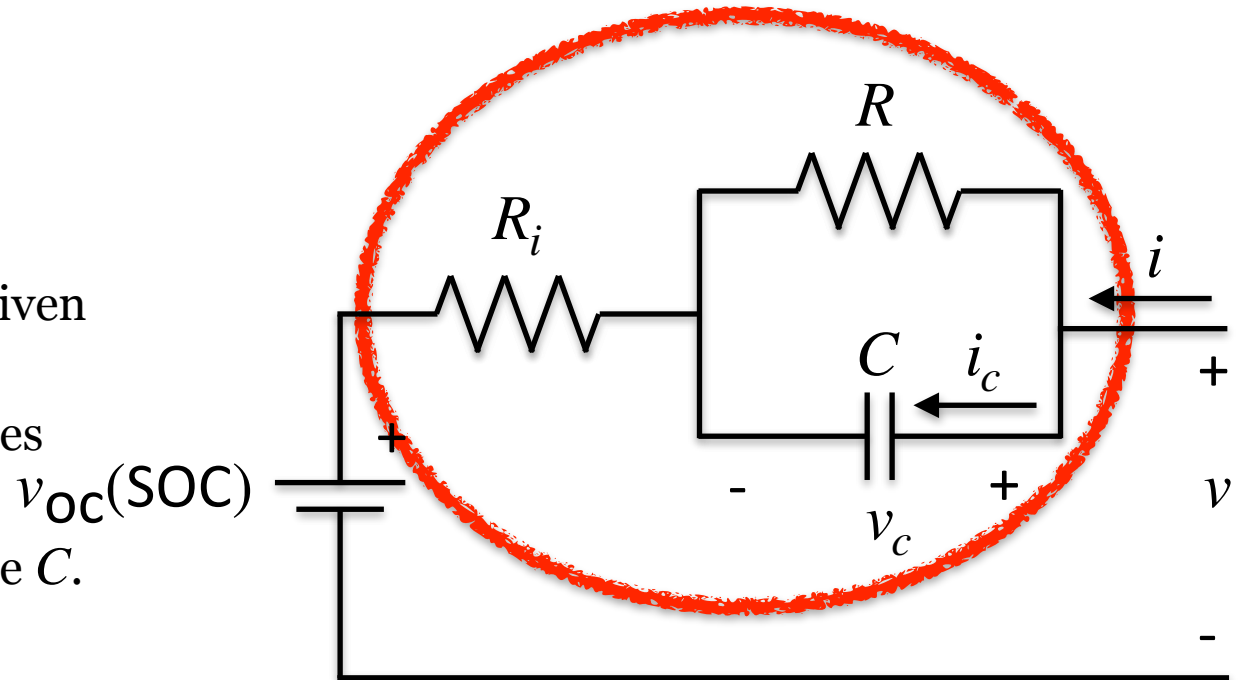


Fundamental Idea for Parameter Identification

1. Set up the battery model so that the voltage $v(t)$ can be estimated from the current

$$\hat{v}(t) = h(i(t) \mid \text{SOC}, R, R_i, C)$$
2. Calculate the parameters so that the model's estimated voltage \hat{v} matches (as closely as possible) the measured voltage v

$$\min_{R, R_i, C} \|v - \hat{v}\|$$

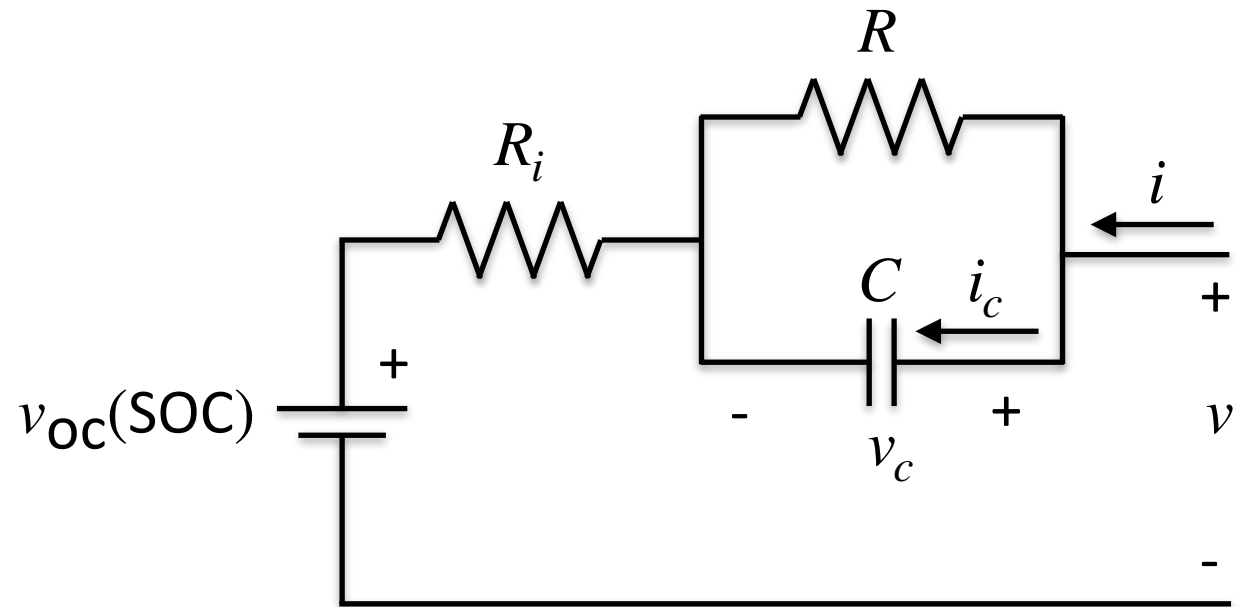RMSE - Root mean square error is one good option



Differential Equations in State-Space Form

Differential equations in the state-space form in continuous-time are written as

$$\frac{dx}{dt} = f(x(t), u(t)) \quad \text{State equation}$$

$$y(t) = g(x(t), u(t)) \quad \text{Measurement equation}$$

Where

- $x(t)$ is the state vector (the variables that are differentiated)
- $u(t)$ the input vector
- $y(t)$ the output vector
- f and g are known often non-linear functions.

If the input signal $u(t)$ for $t \geq 0$ and the initial state $x(0)$ is given the output $y(t)$ for $t \geq 0$ can be computed.

We want to write the battery model in state-space form with $i(t)$ as input and $v(t)$ as output.

Derivation of State-Space Form

Circuit laws give:

$$\text{KVL: } v(t) = v_{\text{OC}}(z) + R_i i(t) + v_c(t) \quad (1) \quad (\text{measurement equation})$$

$$\text{Capacitance: } i_c(t) = C \frac{dv_c}{dt}(t) \quad (2) \quad (\text{state equation for } v_c)$$

$$\text{KVL: } v_c = R(i - i_c) = Ri - Ri_c \quad (3) \quad (\text{used for elimination of } i_c \text{ in (2)})$$

$$\text{SOC: } z = \frac{1}{Q} \int i dt \quad (4) \quad (\text{Can be rewritten as state eq for } z)$$

State-space form:

$$\frac{dv_c}{dt} = -\frac{v_c}{RC} + \frac{i}{C} \quad (5)$$

$$\frac{dz}{dt} = \frac{1}{Q} i \quad (6)$$

$$v(t) = v_c + v_{\text{OC}}(z) + R_i i \quad (7)$$


States: z, v_c

Input: i

Output: v

Constants: R_i, R, C, Q

Function: $v_{\text{OC}}(z)$

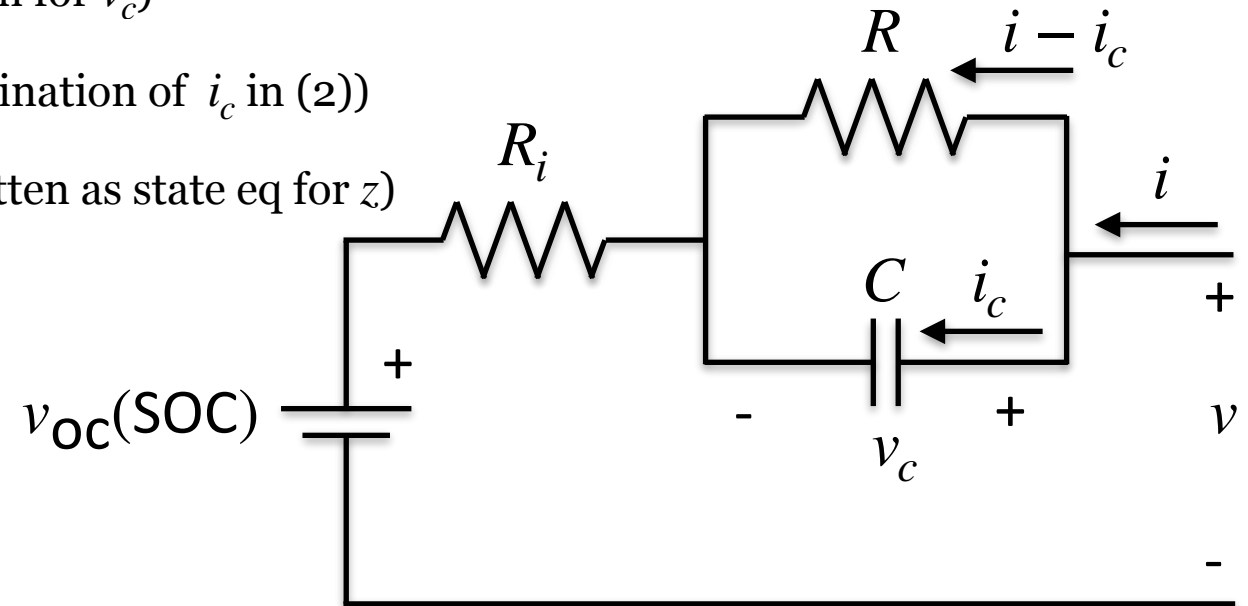

Model Parameters from Current Step Response

Problem Statement

Given the state-space form

$$\frac{dv_c}{dt}(t) = -\frac{v_c(t)}{RC} + \frac{i(t)}{C} \quad (5)$$

$$v(t) = v_c(t) + v_{OC}(t) + R_i i(t) \quad (7)$$



an input $i(t)$ and an initial value of the state $v_c(0)$
the output $v(t)$ can be computed.

Assume a current step:

$$i(t) = \begin{cases} 0 & t < 0 \\ I & t \geq 0 \end{cases}$$

and initial condition $v_c(0) = 0$ V, i.e.,
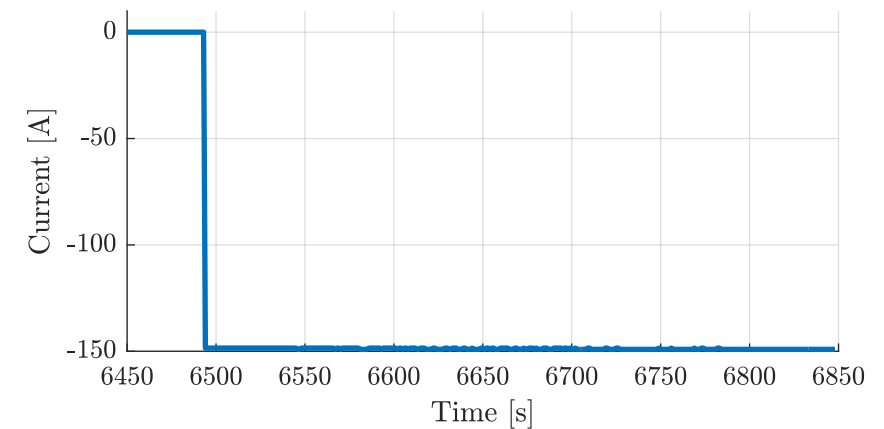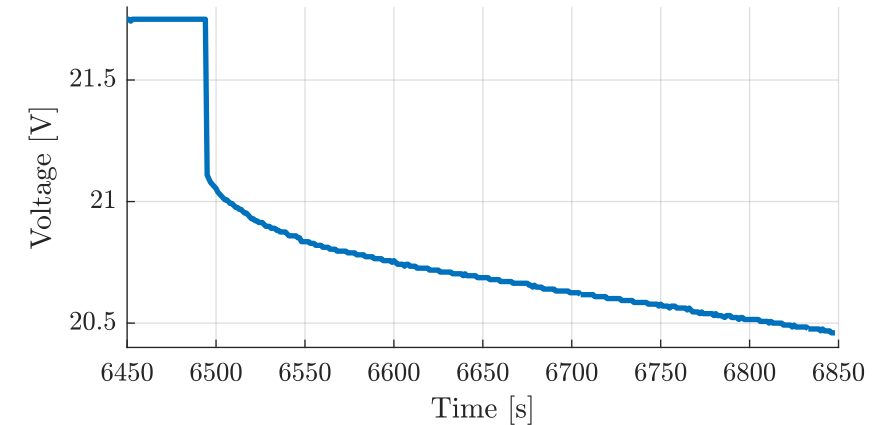
$$v(t) = v_c(t) + v_{OC} + R_i i(t) = v_{OC} \quad \text{f\"or } t < 0$$



Analytical Solution of Differential Equations

An inhomogeneous first-order differential equation is $\dot{y} + ay = f(t)$ and the solution is $y = y_h + y_p$ where $y_h = ke^{-ax}$ and y_p are determined using initial conditions and $f(t)$.

$$\frac{dv_c(t)}{dt} + \frac{v_c(t)}{RC} = \frac{I}{C} \quad (8)$$

The homogeneous solution is $v_{c,h}(t) = ke^{-\frac{t}{RC}}$ and the particular solution is $v_{c,p}(t) = IR$.

$$v_c(t) = v_{c,h}(t) + v_{c,p}(t) \Rightarrow v_c(t) = ke^{-\frac{t}{RC}} + IR$$

The constant k is calculated from the initial condition $v_c(0) = 0$ which gives

$$v_c(0) = ke^{-\frac{0}{RC}} + i(0)R \Leftrightarrow 0 = k \cdot 1 + IR \Leftrightarrow k = -IR$$

This gives the solution


$$v_c(t) = IR(1 - e^{-\frac{t}{RC}}) \quad (9)$$

and if it is substituted into (7), it yields

$$v(t) = \begin{cases} v_{oc} + RI(1 - e^{-\frac{t}{RC}}) + R_i I & t \geq 0 \\ v_{oc} & t < 0 \end{cases} \quad (10)$$

$v(t) = v_{oc} + \underbrace{RI + R_i I}_{\text{constant}}$ as $t \rightarrow \infty \Rightarrow v_{oc}$ decreases due to discharge. Assume a linear decrease

and compensate for this.

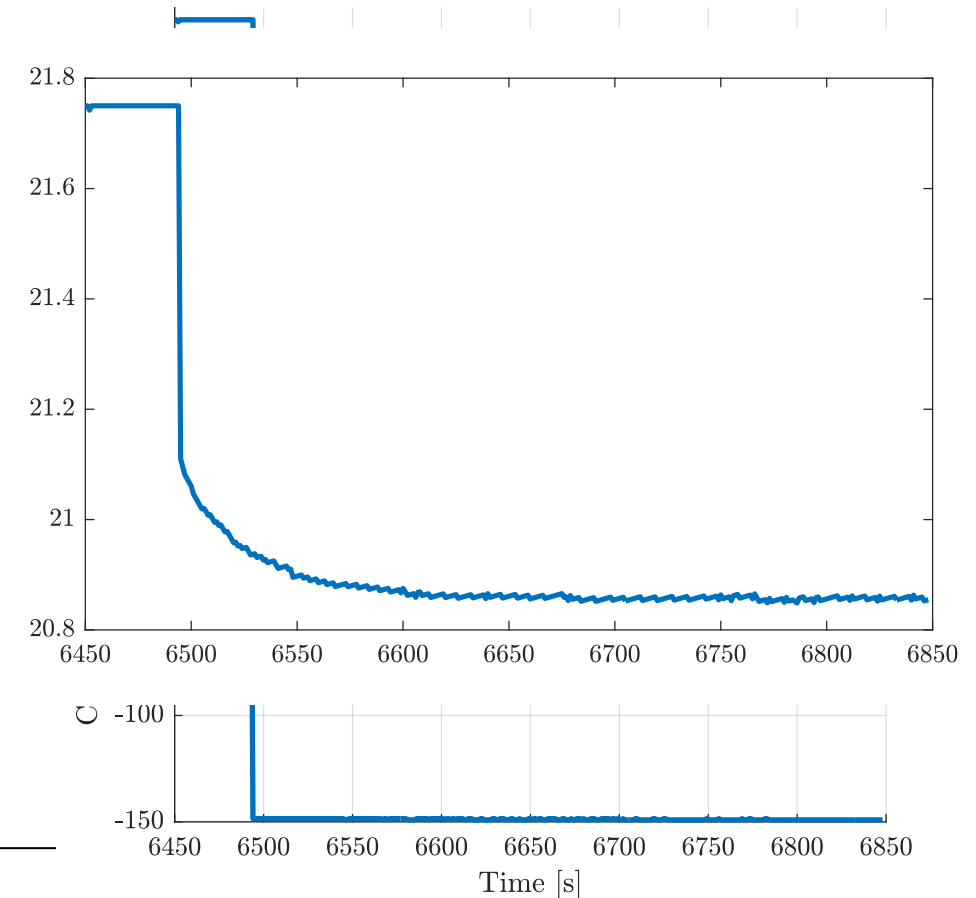

Computation of Model Parameters

v_{oc} : $v(0-) = v_{oc} = 21.75 \text{ V}$

R_i : $v(0) = v_{oc} + IR_i = 21.11 \text{ V}$

$$R_i = \frac{v(t) - v_{oc}}{I} = \frac{21.11 - 21.75}{-149} = 4.3 \text{ m}\Omega$$


R : $v(t) = v_{oc} + I(R_i + R(1 - e^{-\frac{t}{RC}})) \rightarrow v_{oc} + I(R_i + R) \text{ d}\ddot{a} \ t \rightarrow \infty$

$$R = \frac{v(t) - v_{oc}}{I} - R_i = \frac{20.857 - 21.75}{-149} - 4.3 \cdot 10^{-3} = 1.7 \text{ m}\Omega$$

C : The time constant τ for the system is the point in time $t = \tau$ when $1 - e^{-1} = 63 \%$ of the total change of the step response is reached. This gives:

$$\frac{\tau}{RC} = 1 \Leftrightarrow C = \frac{\tau}{R} = \frac{30}{1.7} \text{ kF} = 17.6 \text{ kF}$$
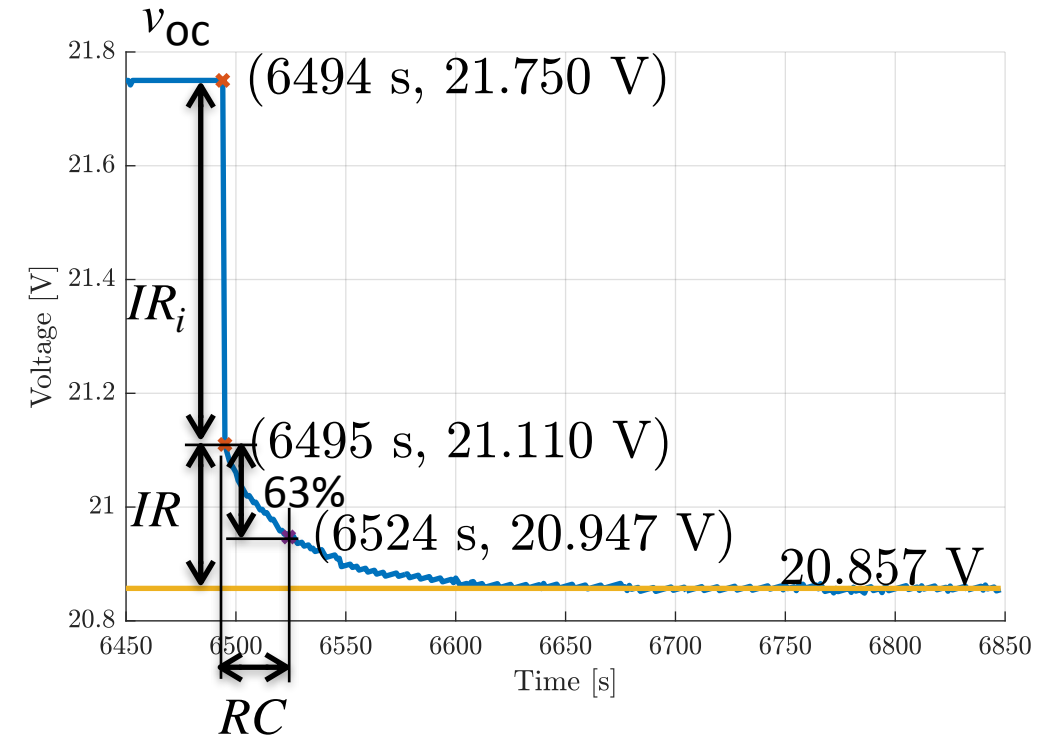
$$v(t) = v_{oc} + I(R_i + R(1 - e^{-\frac{t}{RC}})) \text{ for } t \geq 0$$



Simulation of a time-discretized model

Assume that all signals are sampled at $y(t)$, $y(t + \Delta t)$, $y(t + 2\Delta t)$, ... and denote them y_k , y_{k+1} ,

$$\frac{dv_c}{dt}(t) = -\frac{v_c(t)}{RC} + \frac{i(t)}{C},$$

method)

$$\frac{dv_c}{dt}(t) \approx \frac{v_c(t + \Delta t) - v_c(t)}{\Delta t} = \frac{v_{c,k+1} - v_{c,k}}{\Delta t} \quad (\text{Forward Euler})$$

$$v(t) = v_c(t) + v_{oc} + R_i i(t)$$

Time-discrete model


$$v_{c,k+1} = v_{c,k} \left(1 - \frac{\Delta t}{RC}\right) + \frac{\Delta t}{C} i_k$$

$$v_k = v_{c,k} + v_{oc,k} + R_i i_k$$


```
n = numel(i);    % Input i = [i_1, ..., i_n]'
vc = zeros(n,1); % Initial condition vc(1) = 0
v = zeros(n,1);
for k = 1:n-1
    v(k) = vc(k) + voc(k) + Ri*i(k);
    vc(k+1) = vc(k)*(1-dt/(R*C)) + dt/C*i(k);
end
v(n) = vc(n) + voc(n) + Ri*i(n);
```

How good was the model?

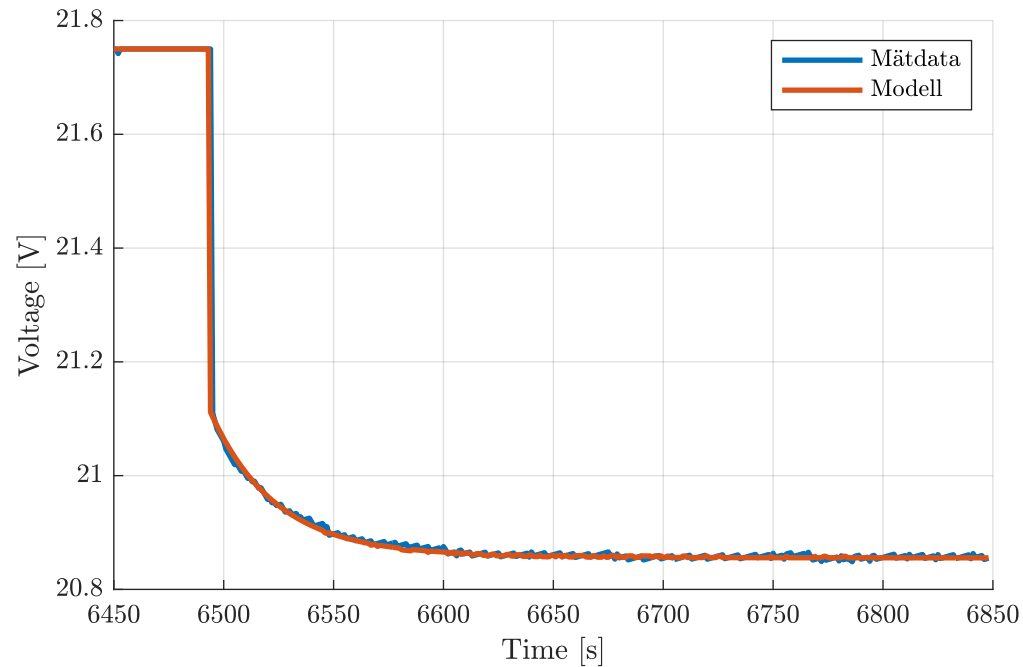The step response with compensation of v_{OC}




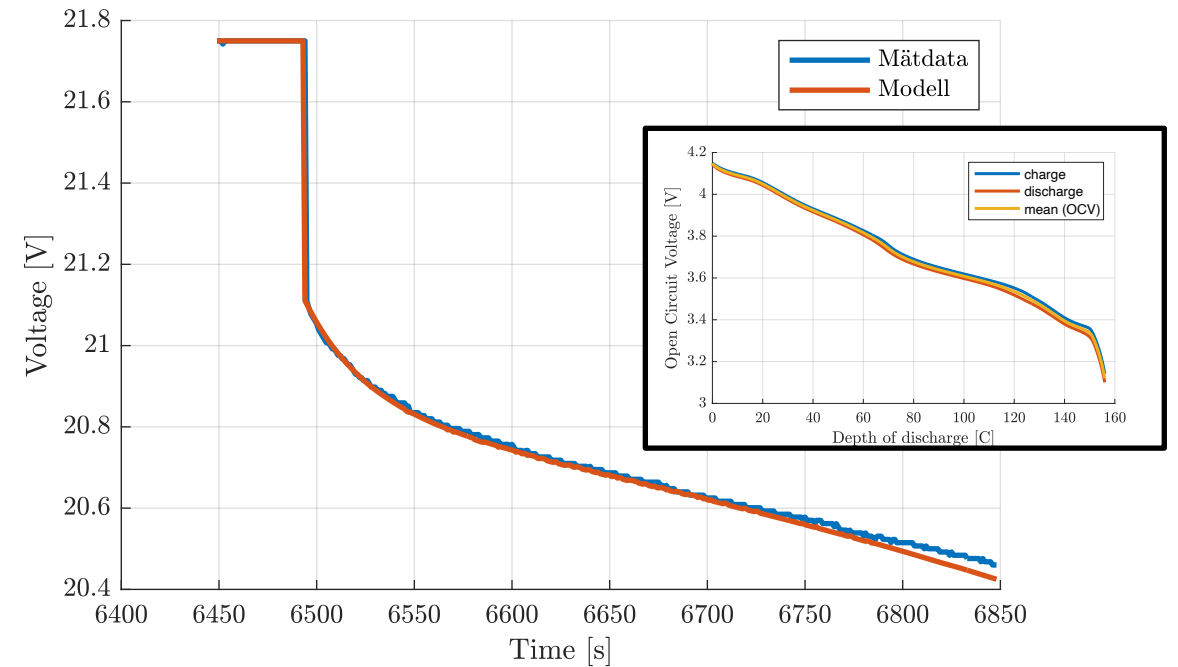
The step response without compensation of v_{OC} but where an estimated OCV curve is used to calculate v_{OC} (DOD)



Model Parameters from Dynamic Operation

Linear Regression for Dynamic Operation

- Consider the data to the left.
- Estimation over a range of different SOC-levels.
- Same problem formulation:
 - Given: $\hat{v}(t) = h(i(t) | \text{SOC}, R, R_i, C)$
 - Find: $\min_{R, R_i, C} \|v - \hat{v}(R, R_i, C)\|$
- Methods
 - Linear regression
 - Non-linear minimization methods.

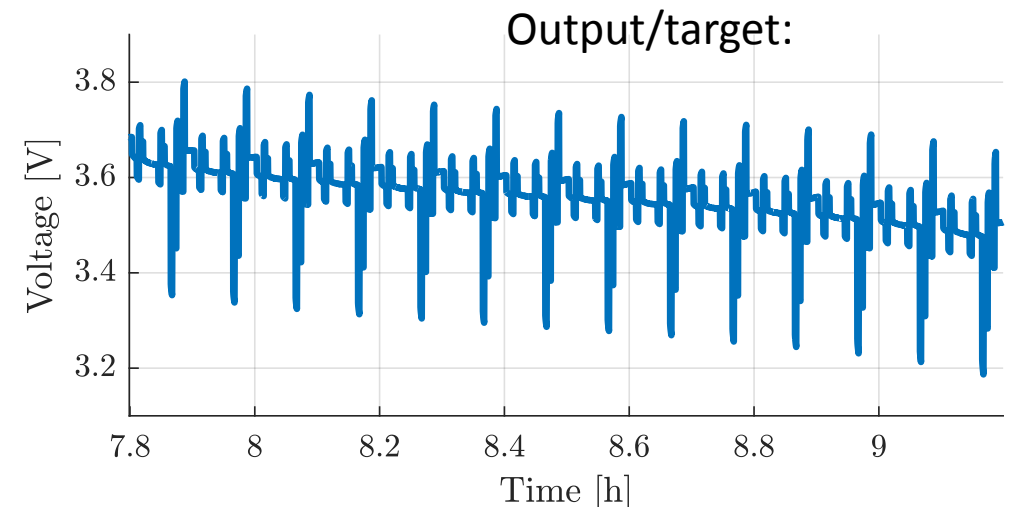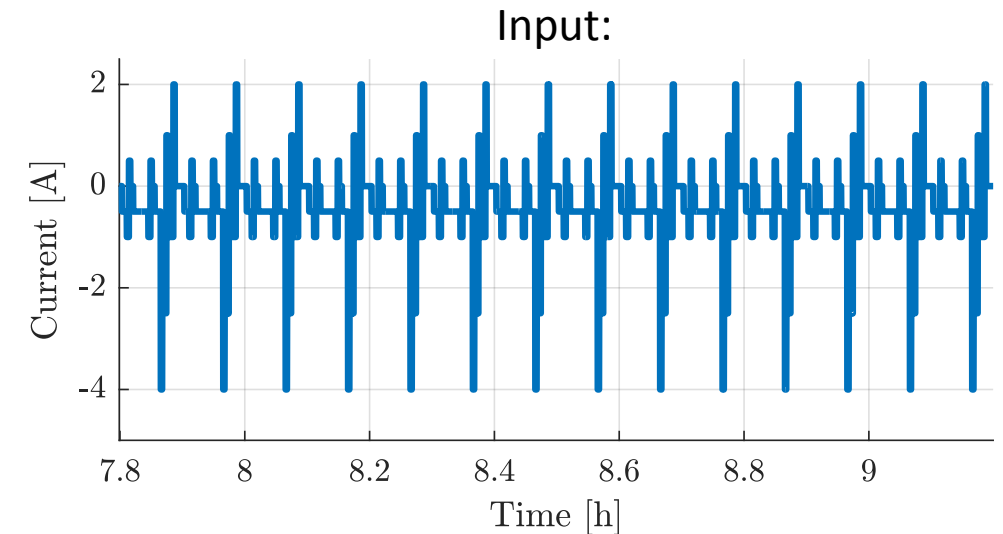


Linear Regression

Linear Regression

- Model equation $Y = X\theta + \varepsilon$ where
 - $Y \in \mathbb{R}^{n \times 1}$: vector of observed outputs
 - $X \in \mathbb{R}^{n \times p}$: matrix of observed inputs
 - $\theta \in \mathbb{R}^{p \times 1}$: parameter vector to be identified
 - $\varepsilon \in \mathbb{R}^{n \times 1}$: error/noise
- Objective:
 - $\hat{\theta} = \min_{\theta} \|Y - X\theta\|^2$
- Closed-form solution
 - $\hat{\theta} = (X^T X)^{-1} X^T Y$ (In Matlab: `Theta = X \ Y;`)
- Model prediction:
 - $\hat{Y} = X\hat{\theta}$

Linear Regression

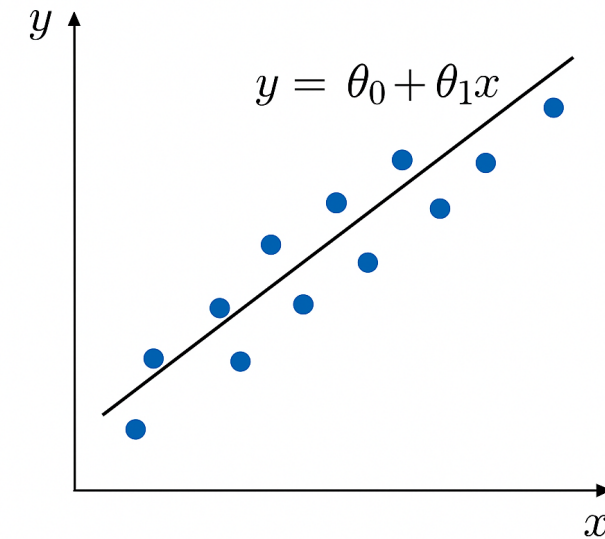

Some Properties

Cons:

- Limited to/assume linear models

Pros:


- Unique solution (if X has full column rank)
- Fast to compute
- Good baseline model

Remove Trend Caused by Changing SOC

- The OCV-function is not linear, but since it has been identified the impedance can be computed using linear regression.
- Alt 1: Use estimated OCV-function and Coulomb-counting

```
n = numel(i); % Insignal v = [v_1, ..., v_n]'
z = SOCf(v(1)); % Initial SOC given by voltage
for k = 1:n-1
    z(k+1) = z(k) + dt * i(k)/Q;
end
v_tilde = v - OCVf(z);
```

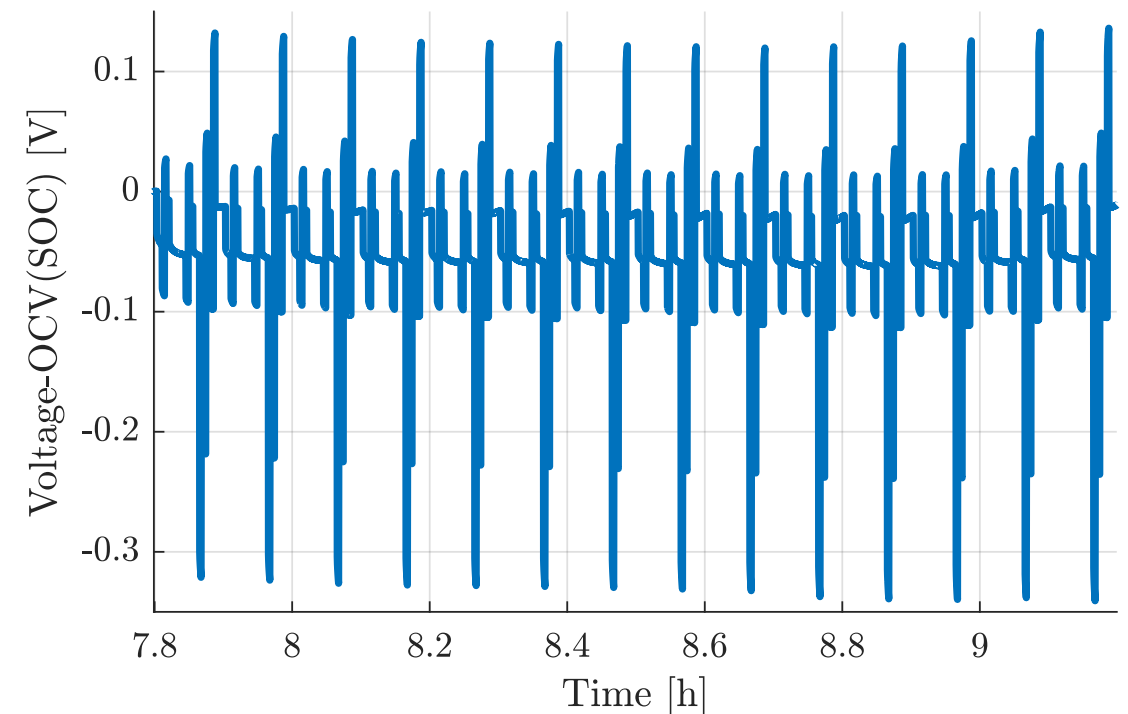- Alt 2: Use a general detrend-function.
- The remaining part is a linear system.



Parameter Estimation using Linear Regression

- $Y = X\theta$ where

$$Y = \begin{bmatrix} \frac{\tilde{v}_2 - \tilde{v}_1}{\Delta t} \\ \vdots \\ \frac{\tilde{v}_n - \tilde{v}_{n-1}}{\Delta t} \end{bmatrix}, X = \begin{bmatrix} \frac{i_2 - i_1}{\Delta t} & -\tilde{v}_1 & i_1 \\ \vdots & \vdots & \vdots \\ \frac{i_n - i_{n-1}}{\Delta t} & -\tilde{v}_{n-1} & i_{n-1} \end{bmatrix}, \text{ and } \theta = \begin{bmatrix} R_i \\ \frac{1}{RC} \\ \frac{R_i}{RC} + \frac{1}{C} \end{bmatrix}$$

In Matlab solved by: `Theta = X\Y;`


Parameters obtained by solving the non-linear equation system:

$$R_i = \theta_1, C = \frac{1}{\theta_3 - \theta_1\theta_2}, \text{ and } R = \frac{\theta_3}{\theta_2} - \theta_1$$

Simulation of Fitted Model

- An example code for simulating the fitted model.
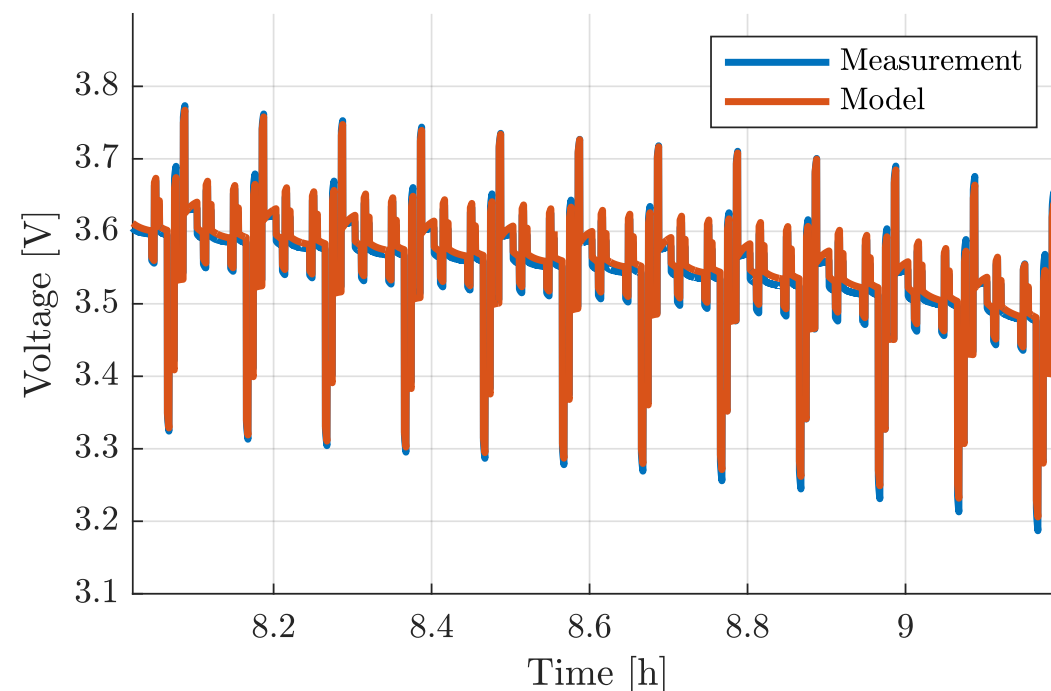
```
n = numel(i); % Insignal i = [i_1, ..., i_n]'
vc = zeros(n,1); % Initial condition vc(1) = 0
z = SOCf(v(1)); % Initial SOC given by voltage
v = zeros(n,1);
for k = 1:n-1
    v(k) = vc(k) + OCVf(z(k)) + Ri*i(k);
    z(k+1) = z(k) + dt * i(k)/Q;
    vc(k+1) = vc(k)*(1-dt/(R*C)) + dt/C*i(k);
end
v(n) = vc(n) + OCVf(z(n)) + Ri*i(n);
```



Non-linear Minimization Methods

Fminunc, $\mathbf{x} = \text{fminunc}(f, \mathbf{x}_0)$. (Unconstrained solver)

Objective: Find the local minimum of a function $f(\mathbf{x})$ with a start in \mathbf{x}_0

- The default solver is the BFGS quasi-Newton method.

Update Rule: $\mathbf{x}_{k+1} = \mathbf{x}_k + \alpha_k \mathbf{p}_k = \mathbf{x}_k - \alpha_k \mathbf{H}_k^{-1} \nabla f(\mathbf{x}_k)$


- \mathbf{H}_k : Approximation of Hessian matrix.
- $\nabla f(\mathbf{x}_k)$: Gradient of the function.
- α_k : Step size (determined by line search)

Summary Workflow

- Compute search direction from gradient and Hessian approximation $\mathbf{H}_k \mathbf{p}_k = -\nabla f(\mathbf{x}_k)$
- Stepsize α_k optimization
- Step update $\mathbf{x}_{k+1} = \mathbf{x}_k + \alpha_k \mathbf{p}_k$
- Hessian approximation update \mathbf{H}_{k+1}

Battery Parameter Estimation by Function Minimisation

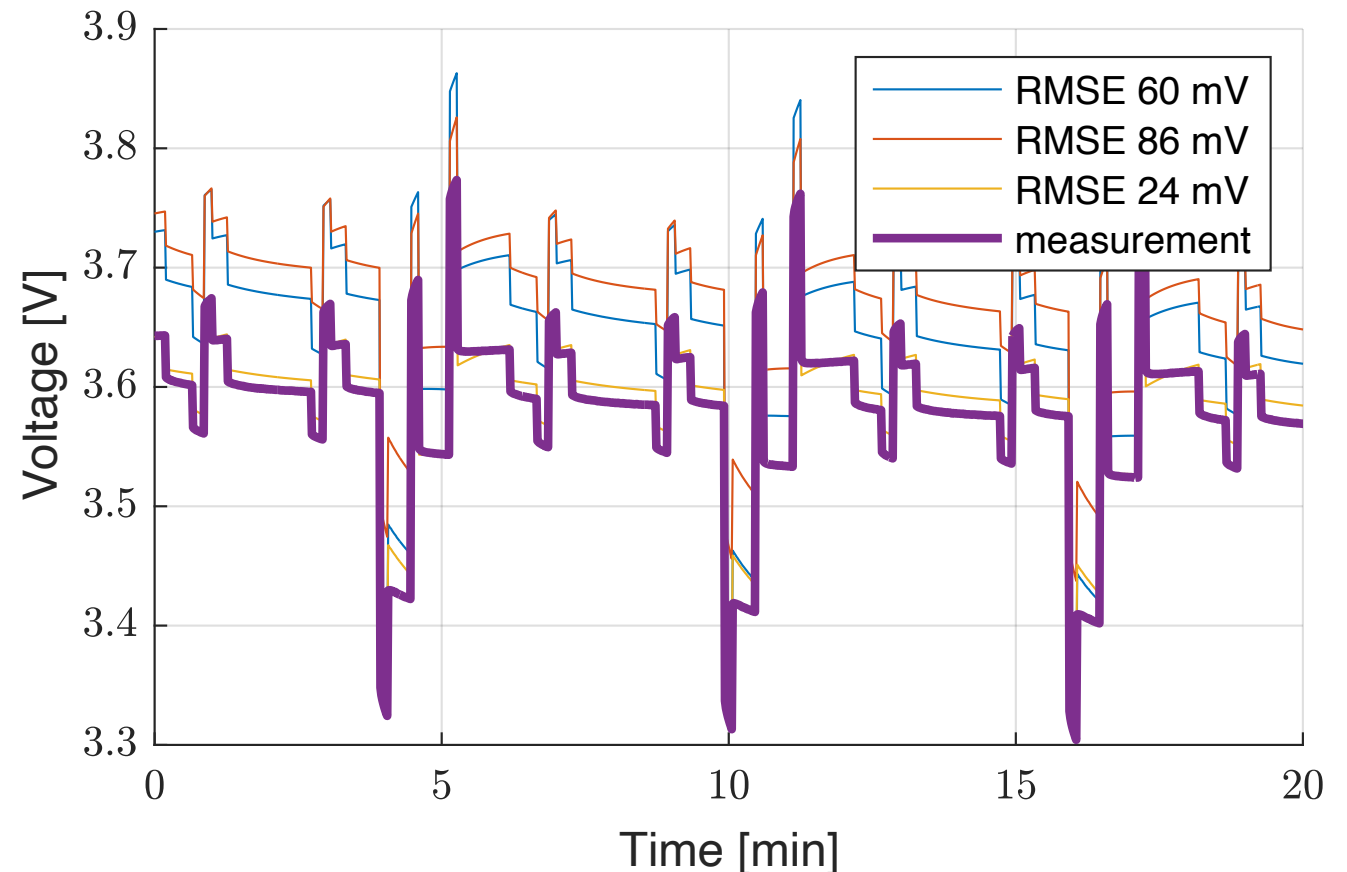- $f(\mathbf{x})$: A scalar measure of model fit.
 - Root Mean Square Estimate (RMSE)
- \mathbf{x} : A vector of the parameters to be estimated.
- Example of simulation with different parameter values.



Define Optimization Function

```
function [r,vhat] = ECM1RC(x,data,OCVf)
```

```
% Init
```

```
v = data.v;
```

```
i = data.i;
```

```
dt = diff(data.t);
```

```
% Set parameters
```

```
Ri = x(1);
```

```
C = x(2);
```

```
R = x(3);
```

```
% Simulate model
```

```
n = numel(i);
```

```
vc = zeros(n,1); % Initial condition vc(1) = 0
```

```
z = SOCf(v(1)); % Initial SOC
```

```
vhat = zeros(n,1);
```

```
for k = 1:n-1
```

```
    vhat(k) = vc(k) + OCVf(z(k)) + Ri*i(k);
```

```
    z(k+1) = z(k) + dt(k) * i(k)/Q;
```

```
    vc(k+1) = vc(k)*(1-dt(k)/(R*C)) + dt(k)/C*i(k);
```

```
end
```

```
vhat(n) = vc(n) + OCVf(z(n)) + Ri*i(n);
```


```
% Evaluate mean square error
```

```
r = mean((v-vhat).^2);
```

```
% Define a function with only  
% parameter values x as input  
fun = @(x) ECM1RC(x,data,OCVf);
```

```
% Find minimizing values
```


```
[x,r] = fminunc(fun,x0)
```

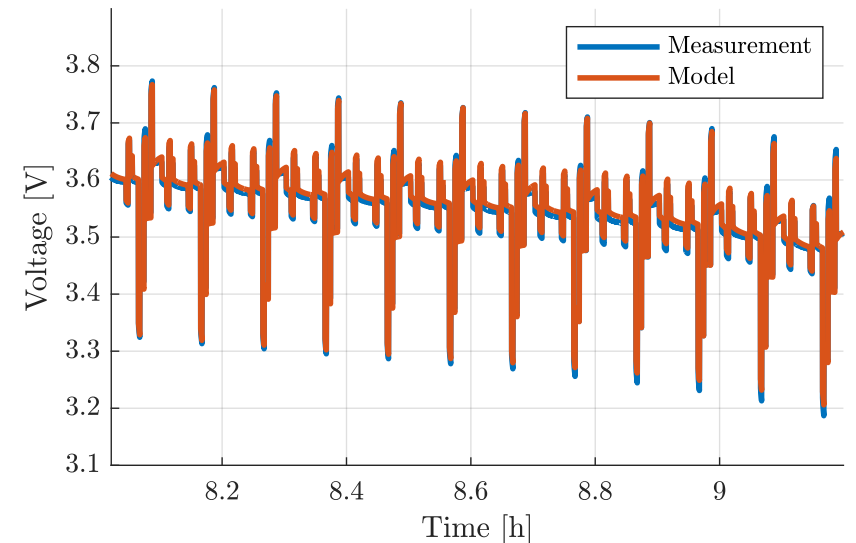


Setting up the Minimization Problem

- Selection of training data

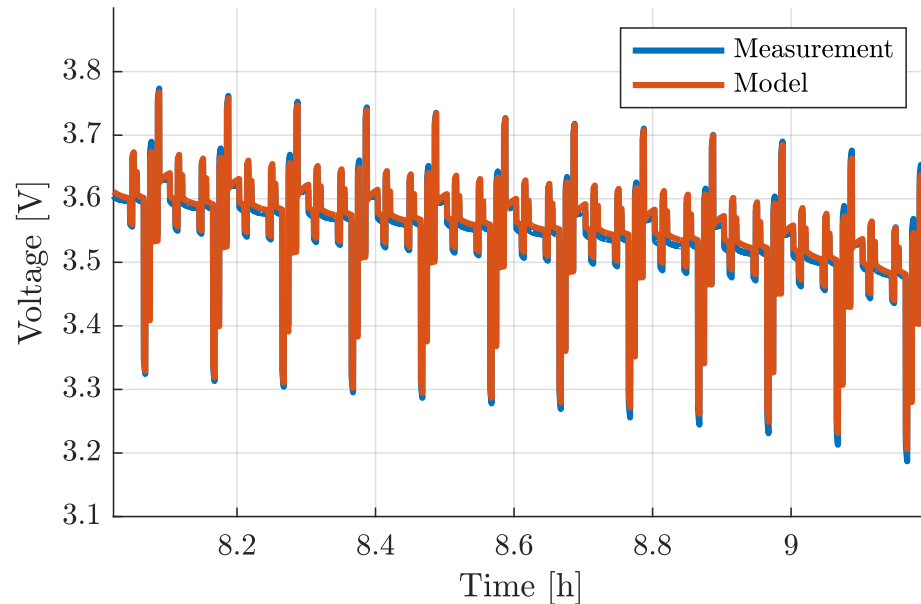High SOC and OCV-function
dependence near fully discharged



Non-deep discharge

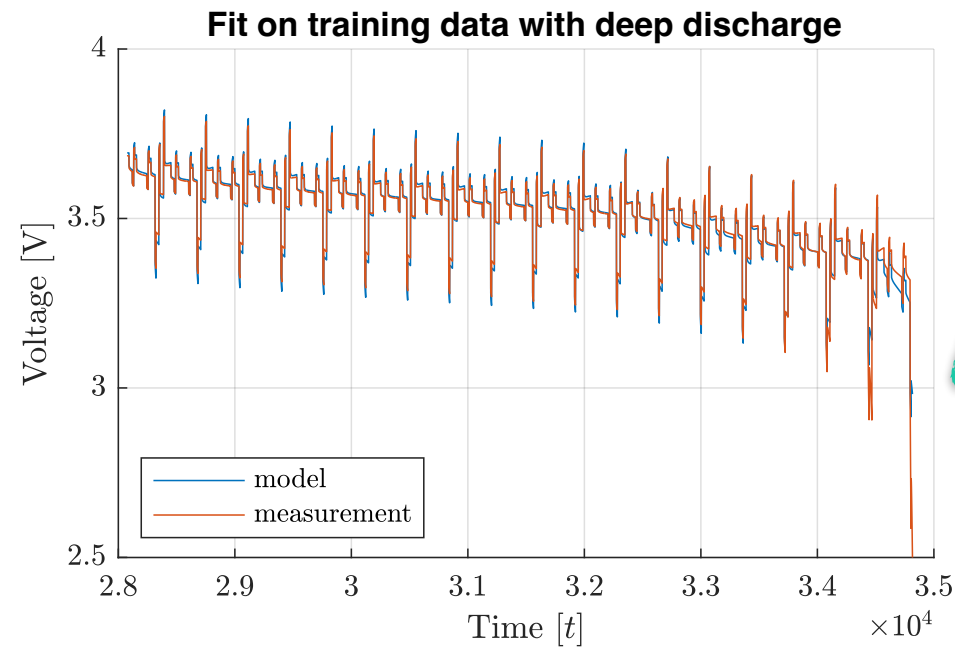

Deep discharge (difficult)

Extending The Parameter Set

With non-linear techniques, it is easy to include, e.g.,

- the initial SOC as an additional parameter to optimize.
- the capacity Q

However, introducing more parameters makes the minimization problem more complex with possible local minima resulting in wrong solutions.


```
% Set parameters
Ri = x(1);
C  = x(2);
R  = x(3);
z  = x(4); % Initial SOC
Q  = x(5);

% Simulate model
n = numel(i);
vc = zeros(n,1); % Initial condition vc(1) = 0
vhat = zeros(n,1);
for k = 1:n-1
    z(k+1) = z(k) + dt(k) * i(k)/Q;
    vhat(k) = vc(k) + OCVf(z(k)) + Ri*i(k);
    vc(k+1) = vc(k)*(1-dt(k)/(R*C)) + dt(k)/C*i(k);
end
vhat(n) = vc(n) + OCVf(z(n)) + Ri*i(n);
```

Why is Initial Guess x_0 Important?

- These methods are local, not global — so they only "see" the landscape near x_0
- A poor initial guess can cause the optimizer to converge to a **bad local minimum**, or even fail to converge.
- A good x_0 (i.e., one near the true minimum) can drastically reduce the number of iterations and function evaluations.

```
[x,r] = fminunc(fun,x0)
```

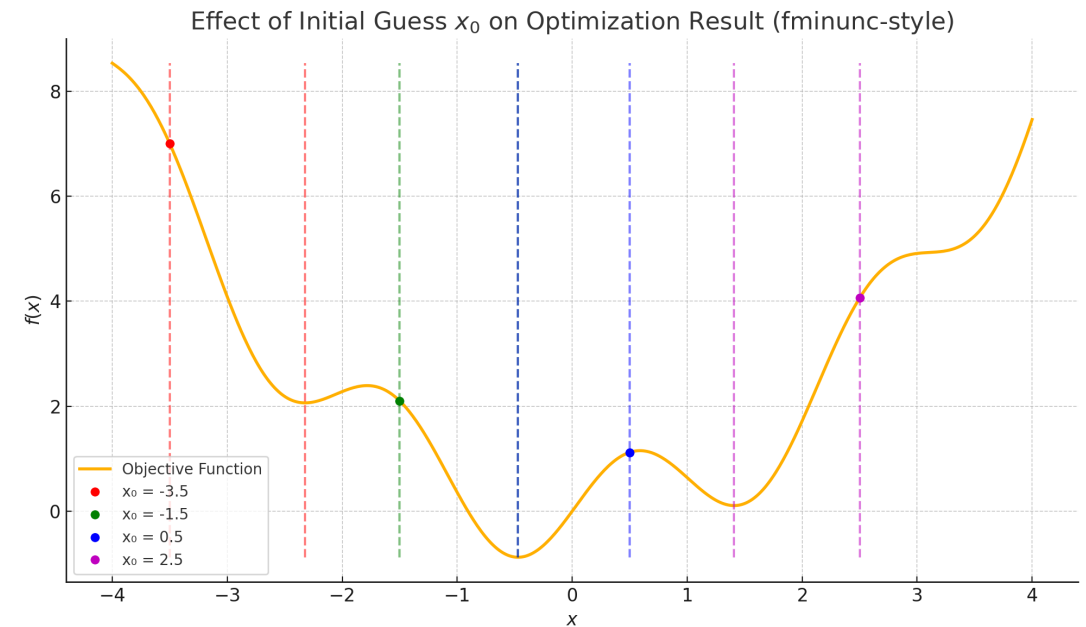

Normalization

- The parameters are of different orders of magnitude, e.g., $R \approx 10 \text{ m}\Omega$, $C \approx 1 \text{ kF}$.
- Normalization is to rescale the parameters to the same size.
- Normalized parameters are easier to optimize with possible improvements in both the speed of convergency and accuracy.
- Implementation:
 - Original problem: $x^* = \arg \min_x f(x)$
 - Assume x_0 is a good guess for $x^* = z \circ x_0$ (elementwise product), then $z_i \approx 1$
 - Solve the normalized problem: $z^* = \arg \min_z f(z \circ x_0)$
 - Recover the original parameters $x^* = z^* \circ x_0$
- Normalization is similar to feature scaling in machine learning.

Lab 1 - Equivalent Circuit Modeling

Lab information

- Register lab groups at [Lisam](#) before Thursday at 16:00.
- Nominal time: 2 + 2 h scheduled sessions
- Lab 1 and 2 will be in Python
- Scheduled in normal classrooms, **work on your laptop**
- Material for lab 1:
 - [Python_installation.md](#) is a quick guide to get started
 - [Instructions](#) with questions to answer
 - [Code skeleton](#) where the tasks are solved by completing the code
 - [Datasets](#) including slow charge cycles and dynamic tests

Learning Outcomes

- **Compute battery capacity** from measurements.
- Compute **open circuit voltage as a function of SOC** from measurement data.
- Convert a time-continuous model into a time-discrete model
- **Compute battery impedance** from
 - A current step using voltage response characteristics.
 - Dynamic operation using
 - linear regression
 - nonlinear minimization techniques
- Describe **experiments** for parameter identification of the different parts of the ECM.

TSFS19 Battery Systems - Lectures 3 and 4

Mattias Krysender

www.liu.se